

*Feature Article:*

## ***How Do Electronic Altimeters Work Part 2***

*Other Features:*

***EMRR Corner***



**Cover Photo: Pemberton  
Technologies Space Ark Jr.  
rocket. To get one, visit:**

[www.ApogeeRockets.com/pemtec\\_space\\_ark.asp](http://www.ApogeeRockets.com/pemtec_space_ark.asp)

Apogee Components, Inc. — Your Source For Rocket Supplies That Will Take You To The “Peak-of-Flight”  
3355 Fillmore Ridge Heights  
Colorado Springs, Colorado 80907-9024 USA  
[www.ApogeeRockets.com](http://www.ApogeeRockets.com) e-mail: [orders@apogeerockets.com](mailto:orders@apogeerockets.com)

## How Do Electronic Altimeters Work - Part 2


Written By Norm Diedzic Jr.

Toward the end of our first installment on altimeters in Newsletter 240 ([www.ApogeeRockets.com/education/downloads/Newsletter240.pdf](http://www.ApogeeRockets.com/education/downloads/Newsletter240.pdf)) it was found that the output of a barometric pressure sensor changes if the supply voltage to the sensor changes. We said this is called ratiometric. With a little thought, it becomes apparent that keeping the supply voltage stable is critical to the operation of an altimeter. If we let this voltage vary, then the signal from our pressure sensor will vary and we won't be able to determine the true altitude.

Since an altimeter needs to be light and portable, the power source of choice is a battery. Batteries come in all sorts of shapes and sizes so there is a nice selection to choose from to power our system. Some altimeters include the mounting for the battery "on-board" the device while

others only have a connector where the modeler wires in their own battery. This is another classic trade off point. With the battery on-board, the altimeter is larger but easier to setup. With the battery off-board, the altimeter is smaller but more complex to install and setup.

Of course with the size of modern electronics, this issue is becoming moot because the entire electronic package for an altimeter can be as small as a battery itself and simple altimeters smaller than a U.S. quarter and powered by coin cell batteries are now available.

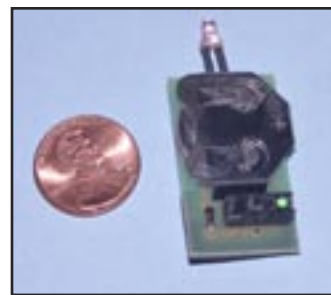


**Figure 3: Mini altimeter and battery board.**

While I haven't seen any altimeters that don't use a battery, I would not be surprised if some time soon, someone will invent one that uses something called a *super capacitor* or *electric double layer capacitor*. These devices have very fast charge and discharge times but not quite the longevity of a battery. However, with the trend to lower power devices, they may well be designed into an altimeter good for a few flights in a super light weight package.


That gives us a lot of battery options but is a battery alone going to give us the nice stable supply voltage required by the barometric sensor? As it turns out, over the useable life of a battery (standard or rechargeable) the voltage drops slowly as the battery's capacity is used up (See Figure 4).

While these curves are relatively flat across the 20% to 80% discharge range, they still slope down to varying degrees across the life of the battery. We need to put something else into our design that will keep give a stable, constant voltage supply for the sensor. What we turn to for this is called a *voltage regulator*.

Voltage regulators take a varying input voltage and make a stable, constant output voltage for use with our electronic components. One of the most popular voltage regulators is the LM317 from National Semiconductor. The

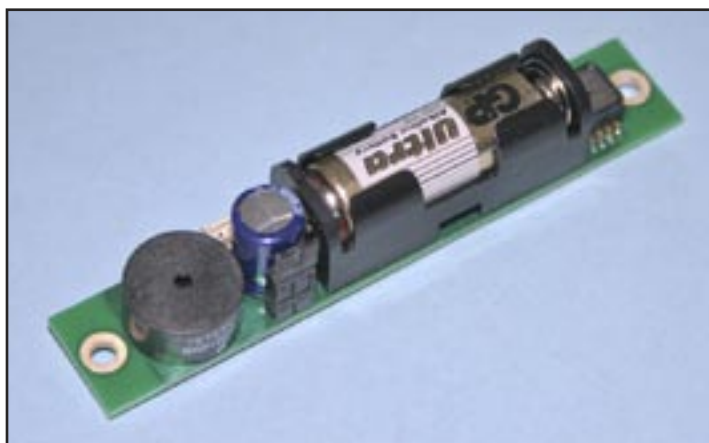

**Figure 1: Altimeter with battery on-board.**

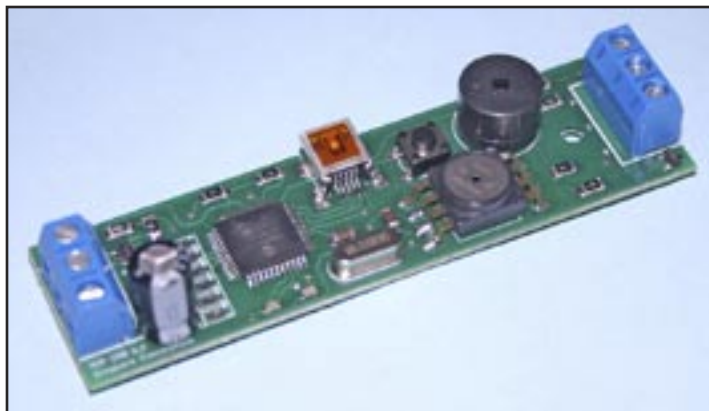

**Figure 2: Altimeter with off-board battery.**

Continued on page 3

### About this Newsletter


You can subscribe to receive this e-zine FREE at the Apogee Components web site ([www.ApogeeRockets.com](http://www.ApogeeRockets.com)), or by sending an e-mail to: [ezine@apogeerockets.com](mailto:ezine@apogeerockets.com) with "SUBSCRIBE" as the subject line of the message.

### Newsletter Staff

**Writer:** Tim Van Milligan  
**Layout / Cover Artist:** Tim Van Milligan  
**Proofreader:** Michelle Mason


Continued from page 2

## How Do Electronic Altimeters Work - 2

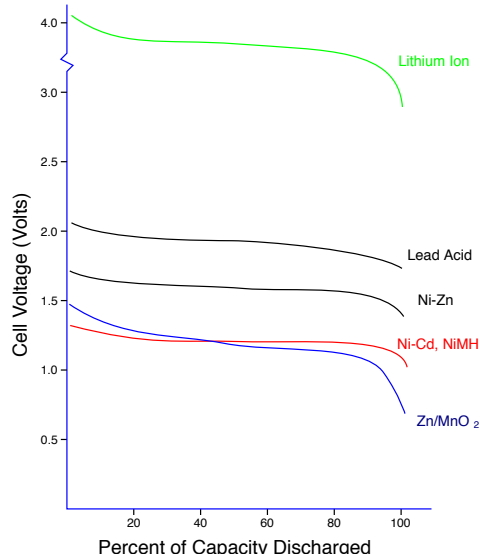

**Figure 4: Battery discharge voltage curves.**

simplified circuit for using the voltage regulator is shown in Figure 5.

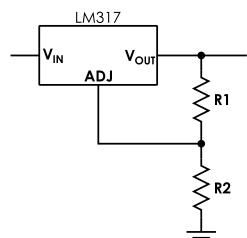


**Figure 5: Simplified regulator circuit.**

$V_{IN}$  is the *un-regulated* voltage coming from the power source or battery and  $V_{OUT}$  is the *regulated* voltage going to the rest of the circuit. R1 and R2 are resistors and the relationship between them determines the regulated output voltage.

The ideal voltage regulator would take any input voltage and supply a constant output voltage to the rest of the system. As usual, nothing is ideal and while the LM317 and regulators like it are great devices, there are some limitations that a designer has to

take into consideration when using them. The first is that you have to supply a higher voltage at the input terminal than you want to get out of the regulator. This extra voltage is referred to as the *dropout voltage* of the regulator. So the input must always be greater than the desired voltage plus the dropout voltage. If the input should drop below this level, the output will start fall as well as shown in Figure 6. This is part of the reason that altimeters are often powered by 9V batteries or mini 12V batteries so that there is enough voltage to allow for the dropout.

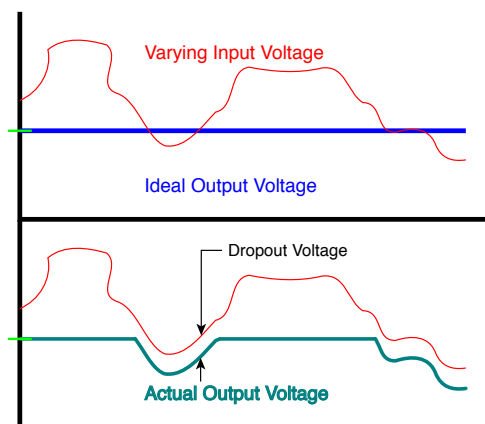

**Figure 6: Ideal vs. Actual Voltage Output.**

Next, they rely on outside components which will have tolerances of their own that must be adjusted for in the final product. This is normally done by replacing one of the resistors with a variable resistor also known as a potentiometer or pot for short. The process of adjusting something during manufacturing is called *calibration*. Older pots are mechanical devices that have a small screw head on them that is turned to adjust the resistance; newer units are all digital and can adjusted by putting voltages on certain pins

Continued on page 4



**ROCKSIM**  
v9

**Your Cool Rocket Designs  
Look So Much Better In  
RockSim Version 9!**

**Launch It.**

**www.RockSim.com**

For further information, call Apogee Components at: 719-535-9335.




Space Foundation certified  
as an excellent teaching aid.






Continued from page 3

## How Do Electronic Altimeters Work - 2

during calibration.

Another issue that comes up with voltage regulation is that the regulator is connected to a varying source on the input side and a varying load on the output side. To compensate for this, it is recommended to put in something called a bypass capacitor on each side of the regulator.

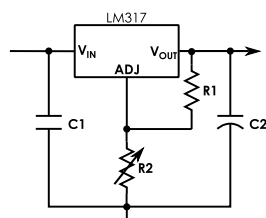


**Figure 7: Standard regulator circuit.**

So our simple regulator circuit becomes more complex. The National Semiconductor datasheet for the LM317 recommends the circuit in Figure 7 for most applications.

The last issue to consider with regulators is power. We need to take into account both how much power the regulator can supply to downstream components as well as how much power the regulator consumes itself.

Our standard LM317 regulator has a dirty little secret in that the more difference between the input and output voltages, the more energy is lost as heat and is of no use

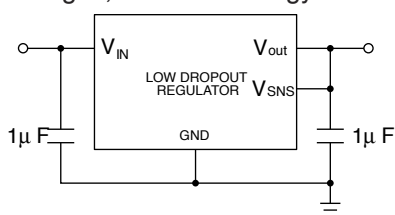

**Figure 8: Typical LDO circuit.**


to us. Newer devices called *Low Drop Out* regulators or LDO's for short are now more common and cost effective. These have lower dropout voltages

and rely on external capacitors instead of resistors so they are more efficient. The trick here is that most of them are designed for a fixed voltage output so they must be selected with the entire system in mind. On the output side, the regulator has to be able to supply enough current to power the downstream devices or the altimeter will fail to do its job.

Next up on our topic list and the subject for the rest of this installment is the *Analog to Digital Converter* or A/D for short. While the concept is rather simple the A/D converters are full of black magic (not really) and a study of them leads to such strange topics as successive approximation, delta sigma conversions, sample and hold, dither and other neat concepts. However, we'll ease into this by discussing the difference between digital and analog signals first.

In the world of controllers, there are two types of signals: *digital* and *analog*. A digital signal can stand for only two states like on or off. Digital signals are used for devices like pushbuttons or key switches or LED lights that are always just on or off. These signals are easy for controllers to handle because they can be represented by a single bit of data. If the bit is zero, then the device is off, if the bit is one then the device is on. At the hardware level, the on state can be signified by a positive voltage and the off state by zero voltage. These voltage levels are generally set for the system. Traditional TTL signals were +5V for on, 0V for off. Newer low voltage devices have different logic levels but the idea is the same.

Continued on page 5

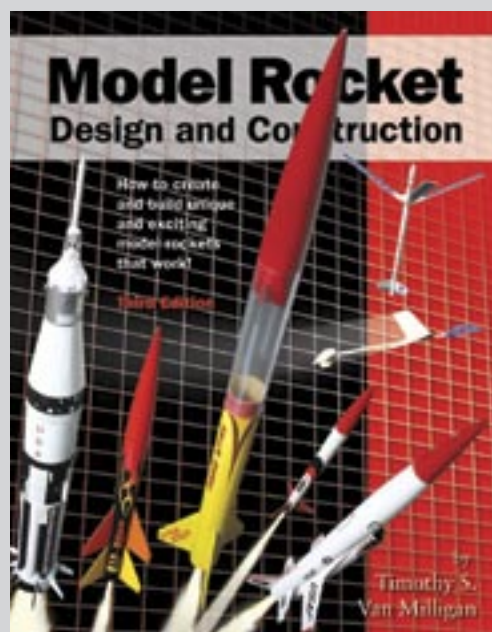

## Model Rocket Design and Construction

By Timothy S. Van Milligan

**New 3<sup>rd</sup> Edition Now Shipping!**

This new 328 page guidebook for serious rocket designers contains the most up-to-date information on creating unique and exciting models that really work. With 566 illustrations and 175 photos, it is the ultimate resource if you want to make rockets that will push the edge of the performance envelope. Because of the number of pictures, it is also a great gift to give to beginners to start them on their rocketry future.

For more information, and to order this hefty book, visit the Apogee web site at: [www.ApogeeRockets.com/design\\_book.asp](http://www.ApogeeRockets.com/design_book.asp)

Apogee Components  
3355 Fillmore Ridge Heights  
Colorado Springs, Colorado 80907 USA

telephone: 719-535-9335  
website: [www.ApogeeRockets.com](http://www.ApogeeRockets.com)

**Apogee**  
COMPONENTS

Continued from page 4

## How Do Electronic Altimeters Work - 2

When it comes to our pressure transducer, theoretically, there are an infinite number of voltages between 0 and the maximum signal voltage designed into the system. This is an analog signal. Analog signals go beyond the on off nature of digital signals and allow us to know the magnitude of the measured value, not just whether it is there or not.

To help understand the difference between digital and analog, think of the difference between a house light on a standard switch and one on a dimmer switch. With the standard (digital) switch, you get light or no light. Those are your only choices. With the dimmer (analog) switch, you can control the brightness of the light from dim to very bright and everywhere in between.

While there is such a thing as an analog computer, for altimeter use, all the controllers used are digital so inside everything has to be a 1 or a 0. We need a way to convert the analog pressure signal into a digital signal that our controller can use to determine the altitude; and that's what the A/D does.

Just because the controller is digital doesn't mean we can't represent numbers larger than 1 within it. True our 1 bit example has only 2 states (0, 1) but if we put 2 bits together, we get 4 possible states (00, 01, 10, 11); with three bits we get 8 possible states (000, 001, 010, 011, 100, 101, 110, 111) and so on... Each time we add a bit, we multiply the number of states by 2. You can also find out the number of states by using the equation  $\text{states} = 2^n$  where n

is the number of bits you are using. This is where all those wonderful computer type numbers like 256 and 1024 come from. ( $256 = 2^8$ ,  $1024 = 2^{10}$ )


When we talk about A/D converters, the first specification we need to know is the *resolution*. This is the number of bits that the A/D uses to represent the analog signal. We speak of an "8 bit A/D" or a "12 bit A/D" and this tells us how fine of a resolution we will have on our signal once it gets converted into a number.

That is a lot of words so let's get moving with an example in round numbers to try to pull all of this together. Say we have a pressure transducer set up in our circuit to output 5 volts at ground level (14.7 psi) and 0 volts at 40,000 ft. (2.7 psi). That's a total *pressure range* of 12 psi.

If I use a very coarse resolution of 3 bits, I get to break my 12 psi up into 8 states. Each state is  $12/8$  or 1.5 psi.

Looking at Figure 9 we see the stair step effect of breaking the signal up into discrete numbers. The red dashed trace is the analog voltage from the sensor. The blue trace shows how the digitized signal changes with pressure.

With this 3 bit example, there are only

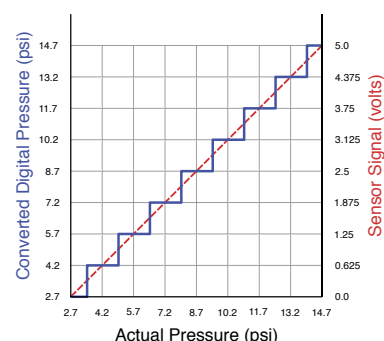

**Figure 9: Analog and digital pressure plot**

Continued on page 6



## Keep Your Reload Cases CLEAN!

Featured Tip on EMRR by Lance Alligood: This method works for all brands and sizes of reloadable motor hardware from 18mm to 98mm. It is particularly useful when you want to use the same casing multiple times at a launch as well as making it easier to do a more thorough clean up when returning home from a launch.

**CLEANING SOLUTION=** 1 part (~16oz) water, 1 part (~16oz) white vinegar, and 1 teaspoon of dish detergent

- 1) Wait until the motor is cool enough to safely handle.
- 2) Disassemble the motor according to the manufacturer's directions/reload instructions. Dispose of the liner and other replaceable items as appropriate.
- 3) Using the CLEANER, liberally spray all of the casings, closures, snap rings, nozzles, etc. and put them in the plastic bucket to soak for at least 5 minutes (but they can soak as long as you like--even till you return home).
- 4) Scrub any parts as necessary with the sponge and/or scrub brush to remove any stubborn residue.
- 5) Repeat steps 3 and 4 if necessary.
- 6) Rinse the parts by spraying them with the WATER bottle.
- 7) Dry parts with paper towels.

Full details and many other tips are found on EMRR!




Brought to you by Essence's Model Rocketry Reviews & Resources - [www.rocketreviews.com](http://www.rocketreviews.com)

## How Do Electronic Altimeters Work - 2

8 possible pressures that can represent the pressure in the controller. Imagining a launch, the controller will see a pressure of 14.7 psi at first and then as the rocket rises, the next number it will see is 13.2 psi. It will have no way of knowing what happens between these two pressures. As we increase the number of bits of resolution, this effect lessens but you can never get rid of it completely. There will always be some of this *stair step* or *digitizing effect* in the converted signal.

So how do these A/D chips go about converting the voltage to a digital number? It turns out that there are several different types of converters. The simplest and also fastest type is called the direct conversion or *flash A/D*. It employs a series of components called *comparators* which each take in two voltages and give a 1 bit output if the test voltage is higher than the reference voltage.

Keeping with our 3 bit example, the schematic for this flash A/D would look like that shown in Figure 10.

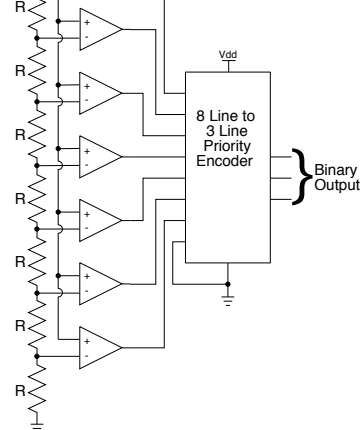

**Figure 10: Flash A/D circuit.**


For our example,  $V_{ref}$  would be 4.375V, then after the first resistor there would be 3.75V and so on down to 0.625V going into the last comparator.

While the flash A/D has the advantage of being very fast (indeed, the conversion happens as fast as the electrons can travel through the circuit), it has the disadvantage of requiring many components. For our 3 bit example, we needed 7 comparators. As we move to larger bit A/D units, the number of comparators is given by the equation  $2^n - 1$  where  $n$  is the bit resolution. So for a minimal 8 bit A/D, we need 255 comparators. This also complicates the encoder section of the A/D circuit.

The number of components required adds cost, size and heat generation to the flash A/D. Larger resolution

flash A/Ds are only used where their speed is absolutely necessary such as video or high quality audio processing equipment.

The next step down the path of the A/D yellow brick road is the *successive approximation A/D* (Figure 11). It only uses one comparator but has the ability to change the comparison reference value with a built in D/A converter.

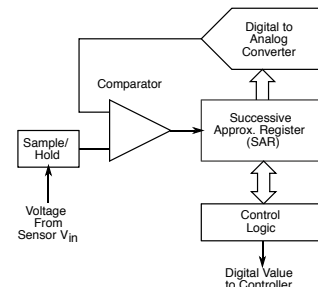

**Figure 11: Successive approximation A/D.**

The name actually gives us a clue to how it works. I like to think of this unit as the “guess a number between 1 and 100” device. It starts by comparing  $V_{in}$  to the middle of the voltage range. If  $V_{in}$  is higher, then it splits the difference and compares it to 3/4 of the range; otherwise it compares it to 1/4 of the range. Note that if  $V_{in}$  is larger than the mid range, the most significant bit will be 1, otherwise it is 0. This dividing continues to “zero in on” the actual voltage setting another bit in the output with each step.

It accumulates these bits in the *Successive Approxima-*

Continued on page 7

## GET THE BEST QUALITY TUBES AT THE BEST PRICE!

### NEW MID-POWER TUBE ASSORTMENT



You get:

- (4) AT 29/13
- (4) AT 41/18
- (2) AT 56/18
- (2) AT 66/18
- (1) AC-56
- (1) AC-66

Price: \$22.72

**You Save: \$5.17**

### THE CLASSIC TUBES-O-PLenty



You get:

- (6) AT 13/18
- (6) AT 18/18
- (6) AT 24/18
- (6) AT 33/18

**Price: \$26.00**

From Estes, you would spend over \$44.45!

**Apogee**  
COMPONENTS

[http://www.ApogeeRockets.com/body\\_tubes.asp](http://www.ApogeeRockets.com/body_tubes.asp)



## How Do Electronic Altimeters Work - 2

tion Register (SAR) and then when finished, outputs the entire word to the controller. The advantage here is you can get whatever bit resolution you want; you just keep dividing voltages until you have enough bits. The disadvantage is that the conversion process takes several steps and the more bits of resolution you want, the longer the conversion takes.

You might wonder what happens if  $V_{in}$  changes while the conversion is taking place? Since the procedure depends on continually comparing a new voltage with the signal voltage, letting the voltage change during the conversion would definitely throw a monkey wrench into the process. These devices have an input section called a *sample and hold* circuit. Its function is to "trap"  $V_{in}$  voltage and hold it constant while the conversion is taking place. This way the A/D is isolated or buffered from changes at the input while the conversion is taking place.

So with the successive approximation A/D we are not required to have a geometrically expanding number of comparators to get higher bit resolutions. We just keep dividing up the voltage between the current approximation and the compared signal to get more and more bits. But nothing is free so what we have traded away for this increased resolution is speed. The more bits of resolution required,

the longer it takes to convert the signal to a digital number. Also, the built in sample & hold and D/A sections of this type of device are a little more complex than the simple comparators and bit encoder of the flash A/D. However, for altimeter use, these types of devices are plenty fast to determine the apogee of a flight or even log points to later plot out the altitude vs. time chart of a launch. Even with an A/D that can look at multiple signals, you can still do 100's of thousands of conversions per second.

The last type of A/D that bears mentioning is the Delta-Sigma (sometimes called Sigma-Delta) A/D. This can also be denoted by  $\Delta\Sigma$  after the Greek letters for Delta and sigma. Figure 12 shows a simplified block diagram for a  $\Delta\Sigma$  converter.

To fully explain the  $\Delta\Sigma$  A/D is beyond the scope of this article but its name comes from the normal use of the Greek symbols in math.  $\Sigma$  or Sigma normally stands for a summing operation while  $\Delta$  or Delta normally denotes the difference between values.

The main parts of this converter are an integrator which performs a *summing*- $\Sigma$  operation, a comparator which looks at the *difference*- $\Delta$  between the sensor voltage and a feedback signal, and a 1 bit A/D converter (I told you there was

Continued on page 8

## Pratt Hobbies GO BOX Launch Controller



- Launch controller for mid-power rockets.
- Hooks right up to your car's battery. No more dead AA batteries!
- Plenty of electricity to set off any type of rocket motor igniter.
- 24 foot cord, allows you to stand far back for launch safety.
- Audible continuity buzzer lets you know the circuit is armed and ready for launch.
- Flat-jaw alligator clips (for easy hook-up of igniter.)



Only  
**\$39.99**

P/N 7705


Brought to you by:

**Apogee**  
COMPONENTS

[www.ApogeeRockets.com/go-box\\_controller.asp](http://www.ApogeeRockets.com/go-box_controller.asp)



## How Do Electronic Altimeters Work - 2

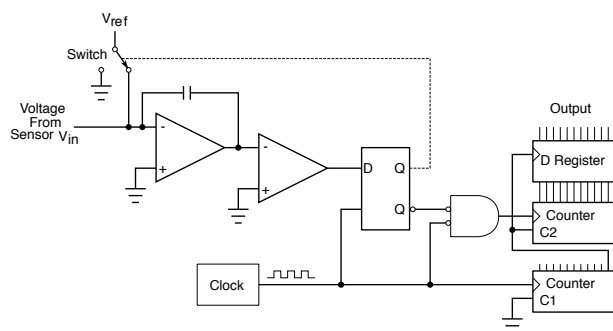

**Figure 12: Delta Sigma A/D**

black magic here).

The obvious question is what good is a 1 bit A/D converter? The first trick here is that the 1 bit A/D converter is only looking at the difference between the current signal and the feedback signal to determine if the signal is raising or falling. While not obvious, these differences get added up by the counter in the block diagram and become the digital number.

The next trick is that a  $\Delta\Sigma$  A/D uses a concept called *oversampling* to run the internal components. So for every digital signal it sends out to the controller, it may have gone through 1000's of cycles internally. This oversampling helps reduce the noise in the signal and allows for a higher

resolution of the output.

You will notice that the  $\Delta\Sigma$  A/D uses very simple components in it and so is very inexpensive to produce. And again, it will be slower than the previous flash and SAR type converts but fine for our rocketry applications. You can easily get 60 samples per second with the  $\Delta\Sigma$  style A/D converter.

If you want a better understanding of the  $\Delta\Sigma$  A/D the last two Bibliography references are a good place to start.


The last point for this article is how these A/D devices communicate their output to the controller. The most basic way is to use an output pin for each bit in the output number. This is called a parallel interface because the traces that connect the A/D with the controller will look like a series of parallel lines.

The problem with this approach is that the pins are usually the most expensive part of an I/C chip and so to get a useable bit resolution we are using a lot of pins. More pins also make the A/D chip larger and heavier which is especially bad for a rocket payload.

A better method is to use a serial communication protocol to move the number between the A/D and the controller. There are a number of standards for this type of interface with names like I<sup>2</sup>c, SPI, CAN and many more. The beauty

Continued on page 9

## High Power Tubes & Couplers

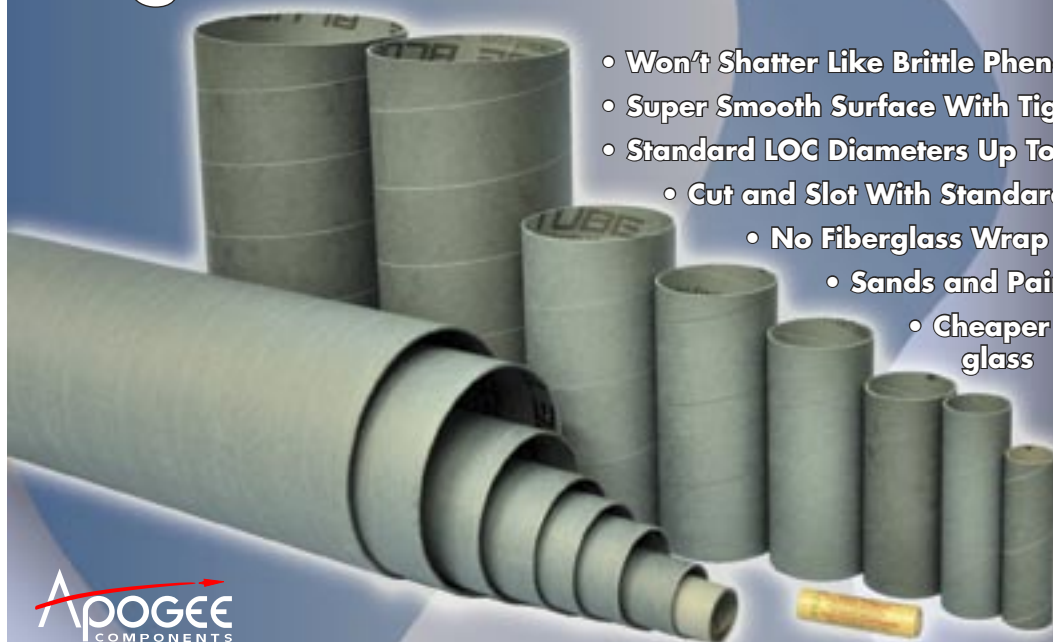

- Won't Shatter Like Brittle Phenolic Tubes!
- Super Smooth Surface With Tight Spirals
- Standard LOC Diameters Up To 6 inches
- Cut and Slot With Standard Tools
- No Fiberglass Wrap Needed
- Sands and Paints Easily
- Cheaper than Fiberglass

Blue Tube From  
Always Ready  
Rocketry

**Apogee**  
COMPONENTS

[www.ApogeeRockets.com/blue\\_tubes.asp](http://www.ApogeeRockets.com/blue_tubes.asp)

[www.ApogeeRockets.com](http://www.ApogeeRockets.com)



## How Do Electronic Altimeters Work - 2

of a serial interface is that it can transmit huge amounts of data over 2 or 4 pins. It does this by sending the data, in our case the sensor voltage converted into a binary number, one bit at a time. The standard interfaces define the speeds, called *bit timings* that the devices use as well as methods of error correction to make sure the numbers sent are received properly.

Some of the standards are *bus interfaces* which allow multiple devices to be connected to the same set of wires for more space and cost savings. Each device on a bus must support the same interface and be set for the same speed and error correction but once they are set up, these busses are great ways to get multiple devices to transmit data.

While we have really just skimmed the surface of these devices you will hopefully have a little better feel for how they work and the sort of decisions that an altimeter designer must make in order to make a working device. Next up we will get to the meat and potatoes of an altimeter and cover the controller that interprets all the data we have been discussing and makes all the decisions.

### Bibliography:

[http://en.wikipedia.org/wiki/Electric\\_double-layer\\_capacitor](http://en.wikipedia.org/wiki/Electric_double-layer_capacitor)

<http://www.mpoweruk.com/performance.htm>

<http://code.rancidbacon.com/LearningHowToPowerCircuits>

LP38690/LP38692 1A Low Dropout CMOS Linear Regulators, National Semiconductor

[http://www.allaboutcircuits.com/vol\\_4/chpt\\_13/4.html](http://www.allaboutcircuits.com/vol_4/chpt_13/4.html)

<http://www.hitequest.com/Kiss/DeltaSigma.htm>

[http://www.maxim-ic.com/appnotes.cfm/an\\_pk/1870/](http://www.maxim-ic.com/appnotes.cfm/an_pk/1870/)

### About The Author:

Norm Diedzic Jr. is an avid rocket flyer and a member of NIRA (Northern Illinois Rocketry Association; NAR Section 117). He has written several technical articles for their LAC winning newsletter, *The Leading Edge*, as well as a treatise on hemispherical parachute construction that appears in the book *Model Rocket Design and Construction*.

You may also recognize Norm as the inventor of a method of restraining small rocket motors in minimum diameter models, called the Dziedzic cut-out method (see *Model Rocket Design and Construction*, 3rd Edition, page 100)

He has an M.S. in Mechanical Engineering from University of Illinois at Chicago, and is currently the Engineering Manager at CMA/Flodyne/Hydradyne, an industrial distribution company serving Northern Illinois and Wisconsin and specializing in hydraulic and electrical motion control.

The advertisement features a blue background with a rocket launch scene on the left. A rocket is shown ascending, with a bright yellow flame at its base. In the foreground, a green circuit board (the Staging Electronics) is shown, connected to a yellow battery pack. The circuit board has various electronic components, including resistors, capacitors, and a small integrated circuit. A yellow wire connects the battery pack to the circuit board. The text 'Staging Electronics' is prominently displayed in large white letters at the top. Below it, a list of features is provided. At the bottom, the website 'www.ApogeeRockets.com/Staging\_Timer.asp' is listed. On the right side, the website 'www.ApogeeRockets.com' is written vertically in blue text. A small note at the bottom left states: 'Battery, battery connector, mounting board and igniter are not included.'

## Staging Electronics

- Designed to ignite the top motor in two-stage rockets.
- Provides an easy way to stage composite propellant motors
- Fires off igniters after a preprogrammed amount of time following liftoff
- G-switch senses liftoff and insures against a false launch-detection
- Small, lightweight design is great for skinny rockets
- Easy-to-use, and will fire off any igniter, including clusters!

Battery, battery connector, mounting board and igniter are not included.

[www.ApogeeRockets.com/Staging\\_Timer.asp](http://www.ApogeeRockets.com/Staging_Timer.asp)

[www.ApogeeRockets.com](http://www.ApogeeRockets.com)